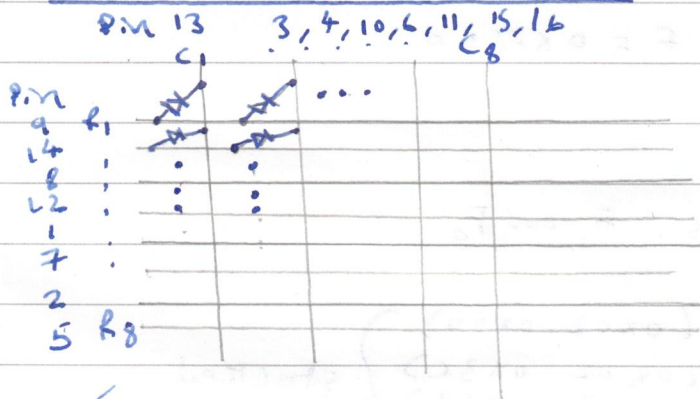


LED matrix with PIC + SIPO

8x8 LED matrix schematic



will need current limiting resistors on either set C or R.

for all off,

$$C = (1 \dots 1) \text{ and } R = (0 \dots 0)$$

use this pin map to connect to the parallel ^{output} data of the 16 bit SIPO register.

let P be the 16 bit parallel output,

$$P = [RC] = [R_1, \dots, R_8, C_1, \dots, C_8]$$

Goal: Drive a 8x8 LED matrix display using a small PIC mc enhanced by SIPO registers.

Block Diagram



Shift Algorithm

Let F be the frame (16 bit) to be displayed,

ser be the serial input,

SCLK be the shift clock, RCLK be the latch

for $i = 0 \rightarrow 16$
ser = $(F \gg i) \& 0x0001$
rising edge on SCLK
latch RCLK

Frames

all off : $F = 0x00ff$

all on : $F = 0xff00$

Letters?

=> Break the image into 8 pieces. F_1, \dots, F_8

i.e.

A :

0	0	0	0	0	0	0	0	$F_1 = (0x01 \ 0x00)$
0	0	X	X	X	X	0	0	$F_2 = (0x02 \ 0x3c)$
0	X	X	0	0	X	X	0	$F_3 = (0x04 \ 0x66)$
0	X	X	0	0	X	X	0	F_4
0	X	X	X	X	X	X	0	F_5
0	X	X	0	0	X	X	0	F_6
0	X	X	0	0	X	X	0	F_7
0	X	X	0	0	X	X	0	$F_8 = (0x0f \ 0x66)$

 } stacked frames.

uint8_t A[8] = { f_1, \dots, f_8 }

This will need 8 cycles (8 complete shifts) to complete the image but will need to be looped to maintain a persistence of vision.

for $i=0 \rightarrow 5$ ^{depends on cycle period and pause period} // persistence
for $k=0 \rightarrow 7$
shift(A[k])

when running on battery, the current limit means that # pixel's brightness depends on the # of on pixels on each image.


The chosen battery must be able to source enough current for a fully lit matrix, for evenly lit images. Also the current limit resistor can be adjusted to make this possible) ? inherent issue?

$$I_{max} = \left(\frac{V_{supply} - V_f}{R_{limit}} \right) \times 8$$

~~limit is shared!~~

✓

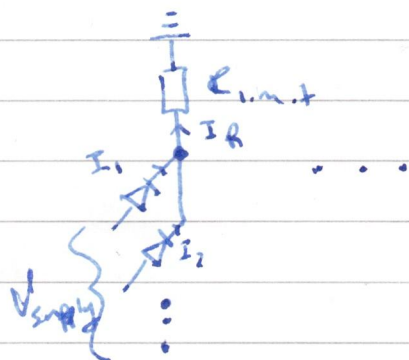R_{limit} shared. so the voltage drop on R_{limit} is still $(V_{supply} - V_f)$




$$KCL: I_R = I_1 + I_2 + \dots + I_n$$

I_R is constant ~~and~~ ~~is therefore~~ and is evenly distributed to all "on" LEDs evenly.

Therefore the brightness of LED depends on the # of LEDs turned on on it's column.

Animation

Rolling text animation:

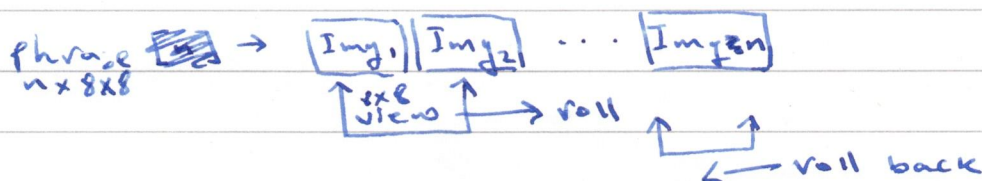

using the bitwise operator \gg and \ll , move the 8x8 wew.

Limitations

\Rightarrow memory: To support all the 52 alphabets (lower + upper)

need $52 \times 8 \times 8 \times 8 = 26,624 \text{ bits} = 3,328 \text{ bytes}$

frame image

Too large.

for small MC, like PIC12F615 which has only 1kb flash.
use bigger MC or external memory IC

\Rightarrow more 8x8 displays: Though adding more displays is trivial as the shift register can be easily chained, the impact this will have on the cycle period maybe too great:

use faster MC.